

EE 210 P – Digital Systems and Design Practicum

Assignment 1


Name : Narmit Kumar

Roll No. : B20218

Branch : Electrical Engineering


Q1.

Ans. Code for AND2 gate:

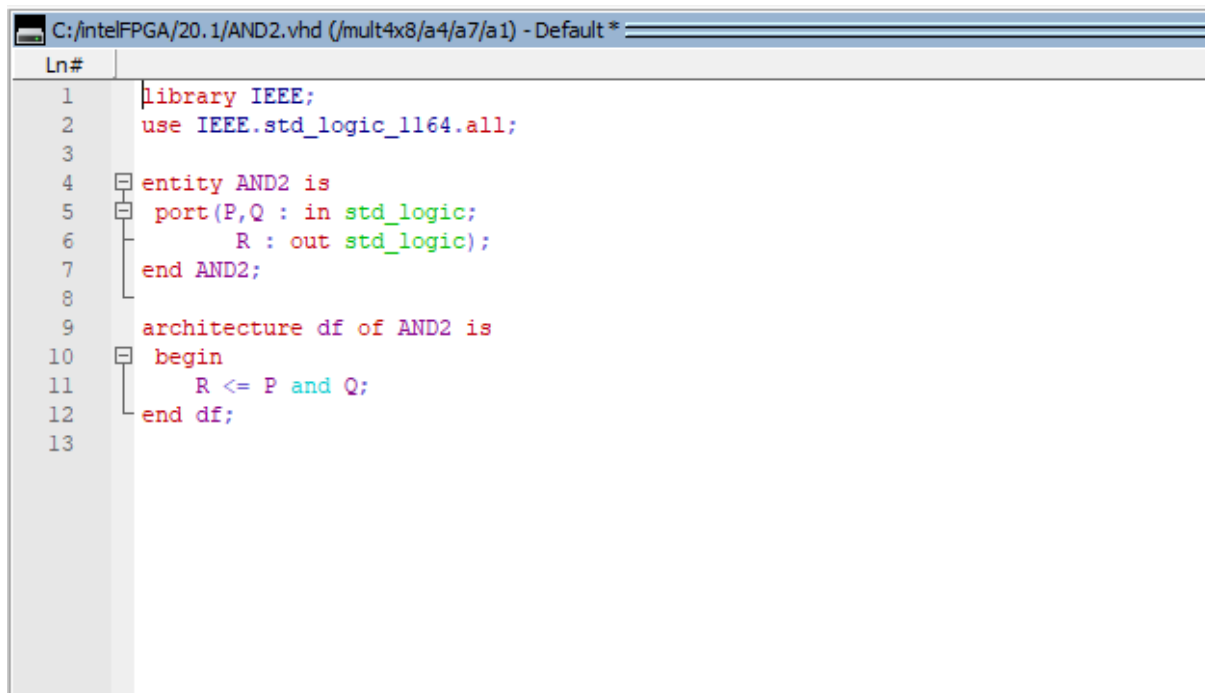

```
C:/intelFPGA/20.1/AND2.vhd (/mult4x8/a4/a7/a1) - Default *  
Ln#  
1  library IEEE;  
2  use IEEE.std_logic_1164.all;  
3  
4  entity AND2 is  
5  port(P,Q : in std_logic;  
6       R : out std_logic);  
7  end AND2;  
8  
9  architecture df of AND2 is  
10 begin  
11     R <= P and Q;  
12 end df;  
13
```

Simulation :

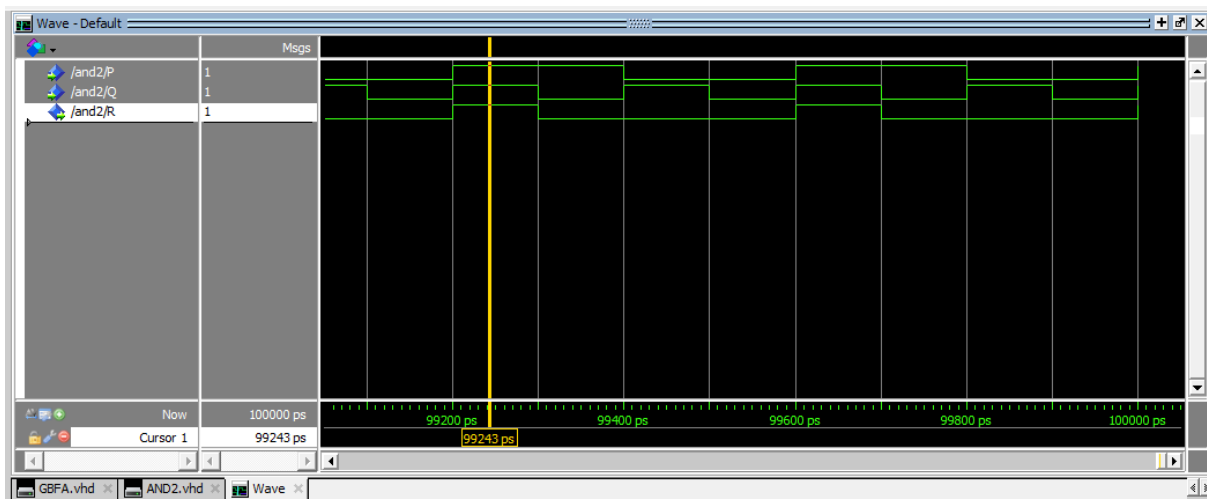


Code for Full Adder circuit:

```
C:/intelFPGA/20.1/FullAdder.vhd (/mult4x8/a4/a7/a2) - Default
library IEEE;
use IEEE.std_logic_1164.all;

entity fa is
port(X,Y,Z : in std_logic;
     U,V : out std_logic);
end fa;

architecture behavior of fa is
begin
    U <= X xor Y xor Z;
    V <= (X and Y) or ((X xor Y) and Z);
end behavior;
```


Simulation :

 

Code for Gated Binary Full Adder (GBFA) :

```
C:/intelFPGA/20.1/GBFA.vhd (/mult4x8/a4/a7) - Default
Ln#
1  library IEEE;
2  use IEEE.std_logic_1164.all;
3
4  entity GBFA is
5  port(A,B,Mgate,Cin : in std_logic;
6       Sout,Cout : out std_logic);
7  end GBFA;
8
9  architecture struct of GBFA is
10 signal Ain: std_logic ;
11 component AND2 is
12 port(P,Q : in std_logic;
13      R : out std_logic);
14 end component;
15 component fa is
16 port( X,Y,Z : in std_logic;
17      U,V : out std_logic);
18 end component;
19 begin
20 a1:AND2 port map(A,Mgate,Ain);
21 a2:fa port map(Ain,B,Cin,Sout,Cout);
22 end struct;
23
```

Simulation:

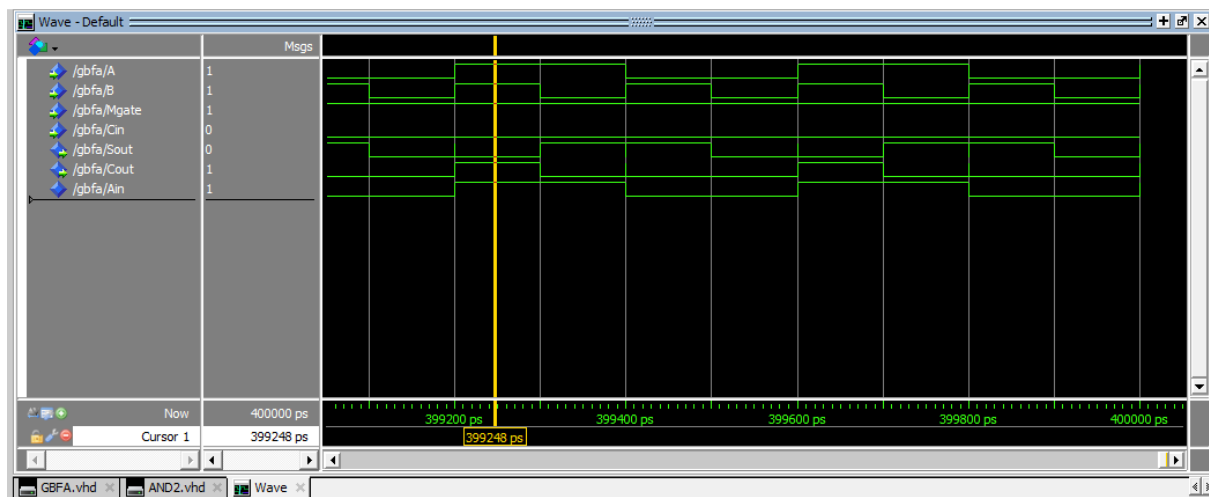


Q2.

Ans. Code for 8-bit Gated binary full adder (G8BFA):

```
Ln#
1  library ieee;
2  use ieee.std_logic_1164.all;
3  entity G8BFA is
4  port(x,y : in std_logic_vector(7 downto 0);
5       Mgate : in std_logic;
6       cin : in std_logic;
7       sum : out std_logic_vector(7 downto 0);
8       cout : out std_logic);
9  end G8BFA;
10
11 architecture datal of G8BFA is
12     signal cary : std_logic_vector(6 downto 0);
13
14     component GBFA is
15     port(A,B,Mgate,Cin : in std_logic;
16          Sout,Cout : out std_logic);
17     end component;
18
19     begin
20
21     a0 : GBFA port map (x(0),y(0),Mgate, cin,sum(0),cary(0));
22     a1 : GBFA port map (x(1),y(1),Mgate, cary(0),sum(1),cary(1));
23     a2 : GBFA port map (x(2), y(2),Mgate, cary(1), sum(2), cary(2));
24     a3 : GBFA port map (x(3), y(3),Mgate, cary(2), sum(3), cary(3));
25     a4 : GBFA port map (x(4), y(4),Mgate, cary(3), sum(4), cary(4));
26     a5 : GBFA port map (x(5), y(5),Mgate, cary(4), sum(5), cary(5));
27     a6 : GBFA port map (x(6), y(6),Mgate, cary(5), sum(6), cary(6));
28     a7 : GBFA port map (x(7), y(7),Mgate, cary(6), sum(7), cout);
29     end datal;
30
```

Simulation:

 

Here, we have added two 8- bit binary numbers 11111000 and 10100000 which gives result 10011000 with a carry 1.

Q3.


Ans. Code :

```

C:/intelFPGA/20.1/Multiplier.vhd (/mult4x8) - Default
Ln#
1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity Mult4X8 is
5  port(A: in std_logic_vector(7 downto 0);
6       B : in std_logic_vector(3 downto 0);
7       Co : out std_logic;
8       P:out std_logic_vector(7 downto 0));
9  end Mult4X8;
10
11  architecture way1 of Mult4X8 is
12  signal q: std_logic_vector(3 downto 0);
13  signal S0,S1,S2,S3,C1,C2,C3,L: std_logic_vector(7 downto 0);
14
15
16
17  component G8BFA is
18  port(x,y: in std_logic_vector(7 downto 0);
19       Mgate : in std_logic;
20       cin : in std_logic;
21       sum : out std_logic_vector(7 downto 0);
22       cout : out std_logic);
23  end component;
24
25  begin
26  L <= "00000000";
27  a1: G8BFA port map(A,L,B(0),'0',S0,q(0));
28  C1 <= q(0)&S0 (7 downto 1);
29  a2: G8BFA port map(A,C1,B(1),'0',S1,q(1));
30  C2 <= q(1)&S1 (7 downto 1);
31  a3: G8BFA port map (A,C2,B(2),'0',S2,q(2));
32  C3 <= q(2)&S2 (7 downto 1);
33  a4: G8BFA port map (A,C3,B(3),'0',S3,q(3));
34
35  P <= (q(3) & "00000000") or ("0" & S3(7 downto 1));
36  Co <= q(3);
37  end way1;
38


```

Simulation :

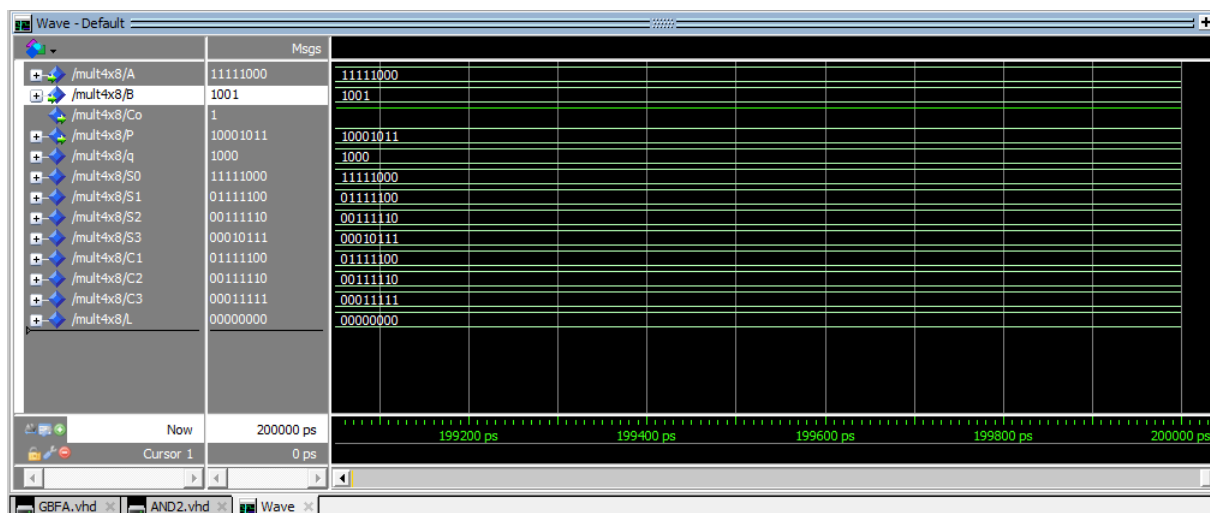

Here , I have multiplied 11111000 with 1001 which gives result 10001011 which is true. Hence , simulation is right.

Another simulation:

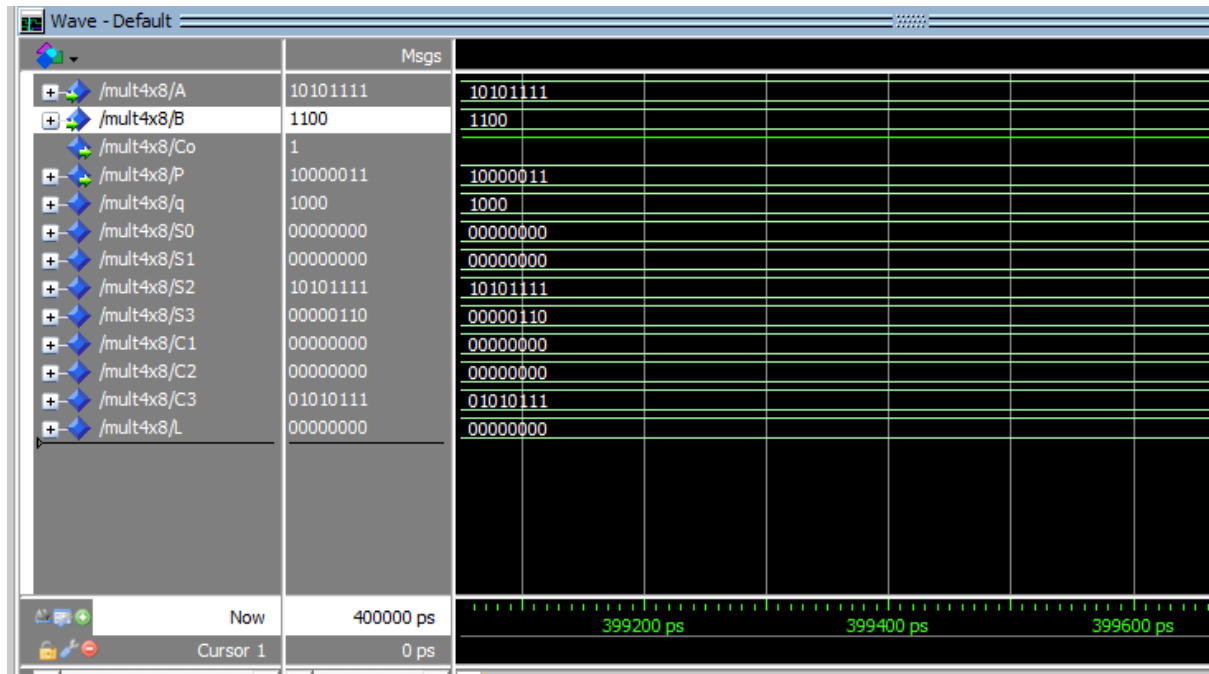

Here , I have multiplied 10101111 with 1100 which gives the true result 10000011. Hence it is correct.